

2-input gates

The AND gate



$$Y = AB$$

$$Y = A \cdot B$$

Truth table:

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

AND operation produces 1
only when A and B are 1.

The OR gate



$$Y = A + B$$

This is "logical addition," written confusingly with '+',

Truth table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

OR produces a 1 when
either or both A or B is
true.

Two interpretations of '+'

arithmetic:

$$1 + 1 = 10_2 \quad (\text{binary})$$

$$1 + 1 = 2_{10} \quad (\text{decimal})$$


logical:

$$1 + 1 = 1$$

Some math texts use $|V| = 1$ for logical addition.
 ↖ "vee"

The AND, OR, and NOT operations are essential to implement logic functions.

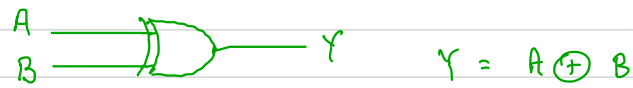Other 2-input gatesThe XOR (exclusive - OR) gate




Truth table

AB	Y
00	0
01	1
10	1
11	0

} produces a 1 if either A or B is 1, but not both.

Each of the AND, OR, and XOR gates also come in inverted form

NAND (NOT-AND)

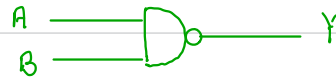

$$Y = \overline{AB}$$

AB	Y
00	1
01	1
10	1
11	0

NOR (NOT-OR)



$$Y = \overline{A + B}$$

AB	Y
00	1
01	0
11	0
10	0

XNOR (exclusive NOT-OR)




$$Y = \overline{A \oplus B}$$

Multiple-input gates

The 2-input gates are also available with 3 or more inputs (to a maximum of 8 in the 7400-series logic gates).

E.g.,

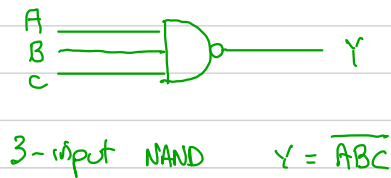


ABC	Y
000	1
001	1
010	1
011	1
100	1
101	1
110	1
111	0

Logic gates as electric circuits


Logic gates operate on binary signals. Logic 1 and 0 are represented by ranges of actual voltages.

Gates themselves are electronic circuits and require an external power supply.

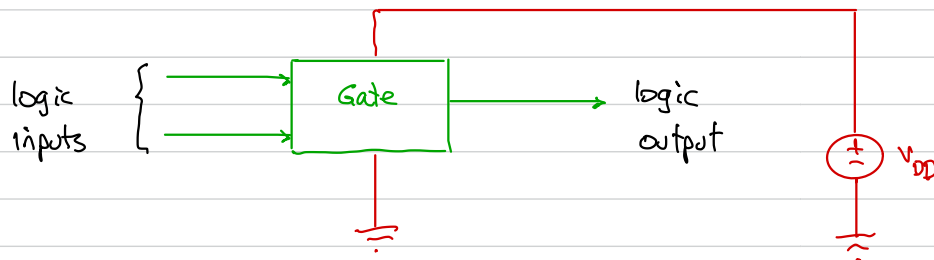


For 7400-series devices, $V_{DD} = 5V$,
More modern devices use V_{DD} as low as 1.2V, or less.

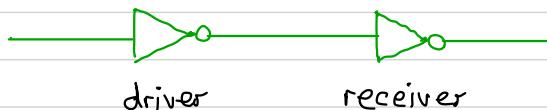
Logic levels: Consider two NOT gates in series



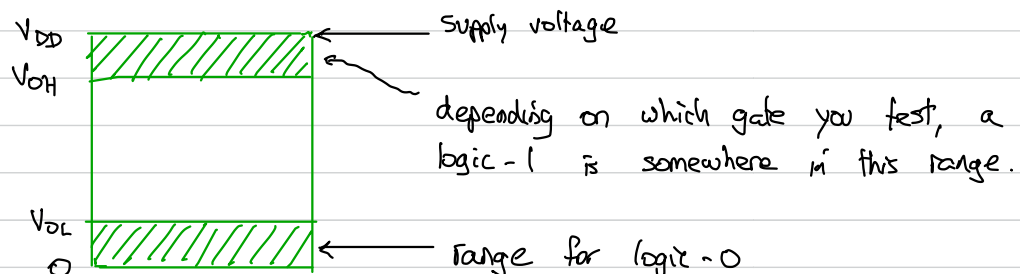Consider the output voltage of the driver



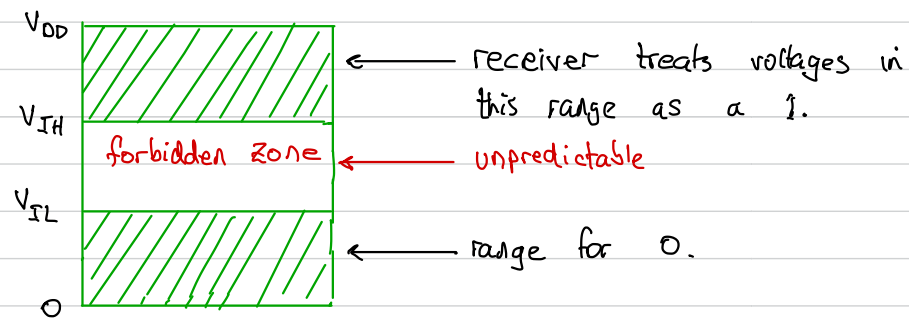Consider the input voltage of the receiver



For the circuit to operate reliably:

$$V_{OH} > V_{IH}$$
$$V_{OL} < V_{IL}$$