

The minimal SOP form

SOP form simplified as far as possible. For function F

- no other SOP expression has fewer product terms
- further, no SOP expression has fewer literals

The expression for Cout determined on Monday is minimal (with 3 product terms, 6 literals).

Another example: comparing 3 equivalent SOP expressions.

$$(1) \quad F = A\bar{B}\bar{C} + A\bar{B}C + ABC \quad \leftarrow (2) \text{ and } (3) \text{ have 1 fewer product term}$$

$$(2) \quad F = A\bar{B} + ABC \quad \leftarrow (3) \text{ has one fewer literal}$$

$$(3) \quad F = A\bar{B} + AC \quad \leftarrow \text{minimal}$$

$$(1) \quad F = A\bar{B}\bar{C} + A\bar{B}C + ABC = A\bar{B}(\bar{C} + C) + ABC$$

$$(2) \quad F = A\bar{B} + ABC = A(\underbrace{\bar{B} + BC})$$


$$\begin{aligned} \text{"add out" } \bar{B} + BC &= (\bar{B} + B)(\bar{B} + C) \\ &= \bar{B} + C \end{aligned}$$

$$(3) \quad F = A\bar{B} + AC$$

We don't yet have an easy way to prove that we have a minimal form.

Drawing schematic diagrams

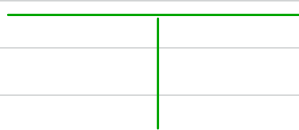Following the conventions in the text, we draw wires this way:



Connection at a
"tee" juncto




Connecting crossing
wires




crossing wires,
no connection

One easy way to draw a circuit

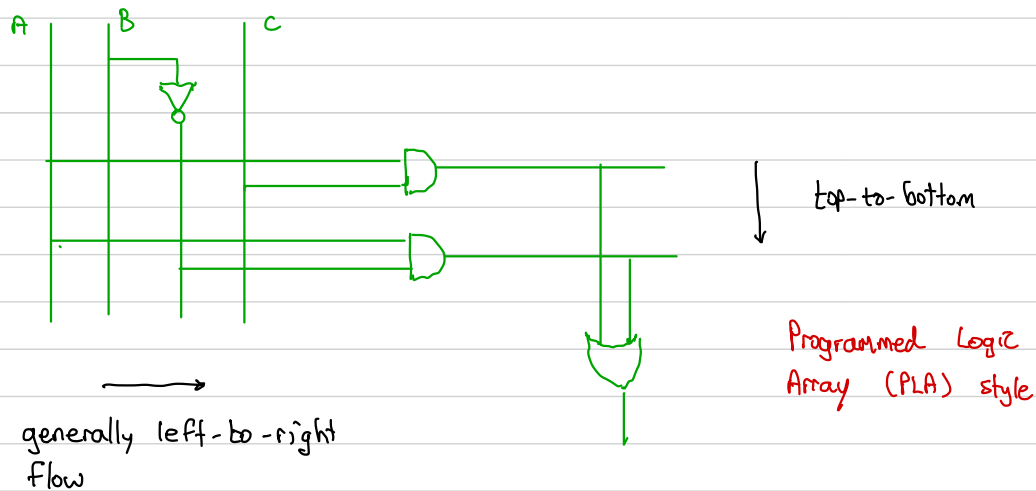

or simply,

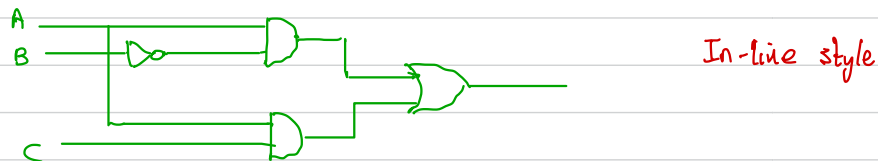

Multilevel combinational circuits

The two circuits above are 2-level circuits

- the NOT gates do not count as a level
- the AND gates here are the first-level gates
- the OR gate is the second-level gate

- naturally suited for any SOP expression

However, 3-or-higher level circuits can reduce hardware requirements

Hardware reduction

For example, following Section 2.5.1 (p.70), the sum bit for a 1-bit full adder