

# Sequential logic design

Vikas Dhiman for ECE275

November 30, 2022

## 1 Objectives

1. Perform a state assignment using the guideline method
2. Reduce the number of states in a state table using row reduction and implication tables
3. Partition a system into multiple state machines

## 2 Full procedure for designing sequential logic circuit

1. Convert the word problem to a state transition diagram. Let the states be  $S_0, S_1, S_2, \dots, S_n$ .
2. Draw state transition table with named states. For example,

Present State	Next State		Outputs	
	X = 0	X = 1	X=0	X=1
$S_0$	$S_1$	$S_2$	0	0
$S_1$	$S_2$	$S_0$	0	0
$\vdots$	$\vdots$	$\vdots$	$\vdots$	$\vdots$

3. State reduction step: Reduce the number of required states to a minimum. Eliminate unnecessary or duplicate states.
4. State assignment step: Assign each state a binary representation. For example,

State name	State assignments ( $Q_2Q_1Q_0$ )
$S_0$	000
$S_1$	001
$\vdots$	$\vdots$

5. Draw State assigned transition table. For example,

Inputs ( $X_1X_0$ )	Present State ( $Q_1Q_0$ )	Next State ( $Q_1^+Q_0^+$ )	Outputs ( $Z_1Z_0$ )
0 0	00	01	0 0
0 0	01	10	0 0
$\vdots$ $\vdots$	$\vdots$	$\vdots$	$\vdots$ $\vdots$

- (a) Use excitation tables to find truth tables for the combinational circuits. For example, the excitation table for J-K ff is

Q	$Q^+$	J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0

### 3 State assignment by guideline method [1, Section 8.2.5]

#### 3.1 State Maps

**Example 1.** Draw a state map for a sequential assignment of the states

 


Figure 8.27 Five-state finite state machine.

#### 3.2 Guideline method

Guideline method states that the following states should be adjacent in the state map according to the following priorities:


 


Figure 8.29 Adjacent assignment priorities.


**Example 2.** A state transition table is given. Find optimal state assignment by using the guideline method.

Input Sequence	Present State	Next State		Output	
		$X=0$	$X=1$	$X=0$	$X=1$
Reset	$S_0$	$S'_1$	$S'_1$	0	0
0 or 1	$S'_1$	$S'_3$	$S'_4$	0	0
00 or 10	$S'_3$	$S_0$	$S_0$	0	0
01 or 11	$S'_4$	$S_0$	$S_0$	1	0

 

**Figure 8.30** Reduced state diagram for 3-bit sequence detector.

 **Example 3.** Draw a Mealy FSM for detecting binary string 0110 or 1010. The machine returns to the reset state after each and every 4-bit sequence. Draw the state transition diagram on your own as practice problem. The state transition diagram is given here. Find optimal state assignment by using the guideline method.



## 4 State reduction by implication chart

**Example 4.** Design a Mealy FSM for detecting binary sequence 010 or 0110. The machine returns to reset state after each and every 3-bit sequence. For now the state transition table is given. Reduce the following state transition table

Input Sequence	Present State	Next State		Output	
		$X=0$	$X=1$	$X=0$	$X=1$
Reset	$S_0$	$S_1$	$S_2$	0	0
0	$S_1$	$S_3$	$S_4$	0	0
1	$S_2$	$S_5$	$S_6$	0	0
00	$S_3$	$S_0$	$S_0$	0	0
01	$S_4$	$S_0$	$S_0$	1	0
10	$S_5$	$S_0$	$S_0$	0	0
11	$S_6$	$S_0$	$S_0$	1	0

## 4.1 Implication chart Summary

The algorithms for state reduction using the implication chart method consists of the following steps

1. Construct the implication chart, consisting of one square for each possible combination of states taken two at a time.
2. For each square labeled by states  $S_i$  and  $S_j$ , if the outputs of the states differ, mark the square with an  $X$ ; the states are not equivalent. Otherwise, they may be equivalent. Within the square write implied pairs of equivalent next states for all input combinations.
3. Systematically advance through the squares of the implication chart. If the square labeled by states  $S_i, S_j$  contains an implied pair  $S_m, S_n$  and square  $S_m, S_n$  is marked with an  $X$ , then mark  $S_i, S_j$  with an  $X$ . Since  $S_m, S_n$  are not equivalent, neither are  $S_i, S_j$ .
4. Continue executing Step 3 until no new squares are marked with an  $X$ .
5. For each remaining unmarked square  $S_i, S_j$ , we can conclude that  $S_i, S_j$  are equivalent.

## References

- [1] Randy Katz and Gaetano Barriello. *Contemporary Logic Design*. Prentice Hall, 2004.

Ask for reference PDF if you need it.