

Homework 4

Max marks: 40

Due on Oct 1st, 2021, 9 AM, before class.

Problem 1 Hazard problem: Design a hazard free SOP for $f(A, B, C, D) = \sum m(0, 1, 4, 5, 6, 7, 9, 11, 14, 15)$

$$f = hx_1 + \bar{h}\bar{x}_1 \quad (1)$$

$$= \bar{x}_1 \oplus h \quad (2)$$

$$= \bar{x}_1 \oplus (x_3 \oplus x_4) \quad (3)$$

Solution

The K-map for f is

		\bar{A}	A	
		\bar{B}	B	\bar{B}
\bar{C}	\bar{D}	1	1	0
	D	1	0	1
C		0	1	1
	\bar{D}	0	1	0

$$f = \bar{A}B + BC + ACD + \bar{A}\bar{C} + A\bar{B}D + \bar{B}\bar{C}D$$

Cost(f) = 6 AND gates + 2*3 + 3*3 inputs to AND gates + 1 OR gate + 6 inputs = 28.

Problem 2 Find the simplest realization of the function $f(x_1, \dots, x_4) = \sum m(0, 3, 4, 7, 9, 10, 13, 14)$, assuming that the logic gates have a maximum fan-in of two.

Solution

The K-map for f is

		\bar{x}_1	x_1	Row pattern
		\bar{x}_2	x_2	\bar{x}_2
\bar{x}_3	\bar{x}_4	1	1	0
	x_4	0	0	1
x_3		1	1	0
	\bar{x}_4	0	0	1
Col pattern		\bar{h}	\bar{h}	h

Writing f in terms of column pattern $h = \bar{x}_3x_4 +$

Cost(f) = 2 XOR gates + (2+2) inputs each = 6. Max fan-in = 2.

Problem 3 Find the minimum-cost circuit for the function $f(x_1, \dots, x_4) = \sum m(0, 4, 8, 13, 14, 15)$. Assume that the input variables are available in uncomplemented form only. (Hint: Use functional decomposition.)

Solution

The K-map for f is

		\bar{x}_1	x_1	Row pattern
		\bar{x}_2	x_2	\bar{x}_2
\bar{x}_3	\bar{x}_4	1	1	0
	x_4	0	0	1
x_3		0	0	1
	\bar{x}_4	0	0	1
Col pattern		$h = \bar{x}_3\bar{x}_4$	h	\bar{h}

Write f in terms of g ,

$$f = \bar{x}_3\bar{x}_4\bar{g} + \bar{x}_3\bar{x}_4g \quad (4)$$

$$= \bar{x}_3 + \bar{x}_4\bar{g} + \underbrace{(x_3 + x_4)}_{h_2}g \quad (5)$$

$$= \bar{h}_2\bar{g} + h_2g \quad (6)$$

$$= \bar{h}_2 \oplus g \quad (7)$$

$$= (\bar{x}_3 + \bar{x}_4) \oplus (x_3 + x_4) \quad (8)$$

Cost(f) = 1 OR gate + 2 inputs for OR gate + 1 AND gate + 2 inputs for AND gate + 1 XOR gate + 2 inputs for XOR gate + 1 NOT gate + 1 input to NOT gate = 11.

Problem 4 Use functional decomposition to find the best implementation of the function $f(x_1, \dots, x_5) = \sum m(1, 2, 7, 9, 10, 18, 19, 25, 31) + D(0, 15, 20, 26)$. How does your implementation compare with the lowest-cost SOP implementation? Give the costs.

Solution

The K-map for f is given in Table 1.

We try writing $\bar{x}_1 = 1$ half of f in terms of Row patterns $g = x_3$, and $x_1 = 1$ half of f in terms normal K-map grouped terms,

$$\begin{aligned} f &= \bar{x}_1 \left(\underbrace{(\bar{x}_4 x_5 + x_4 \bar{x}_5)}_h \bar{x}_3 + \underbrace{x_4 x_5}_{h_2} x_3 \right) \\ &\quad + x_1 \bar{x}_2 \bar{x}_3 x_4 + x_2 x_3 h_2 + x_2 \bar{x}_3 h \\ &= \bar{x}_1 h \bar{x}_3 + \bar{x}_1 h_2 x_3 + x_1 \bar{x}_2 \bar{x}_3 x_4 + x_2 x_3 h_2 \\ &\quad + x_2 \bar{x}_3 h \end{aligned}$$

Cost(h) = 1+2=3. Cost(h_2) = 1+2=3. Total Cost of f = Cost(h) + Cost(h_2) + 5 AND gates + 4*3 input per gate + 4 inputs to AND gates + 1 OR gate + 5 inputs = 3+3+5 + 12+4+1+5=33.

Normal grouping is shown in Table 2.

$$\begin{aligned} f &= \bar{x}_3 x_4 \bar{x}_5 + x_1 \bar{x}_3 \bar{x}_4 \bar{x}_5 + x_1 x_3 x_4 x_5 \\ &\quad + x_1 \bar{x}_2 \bar{x}_3 x_4 + x_2 x_3 x_4 x_5 + x_2 \bar{x}_3 \bar{x}_4 x_5 \quad (9) \end{aligned}$$

Cost(f) = 6 AND gates + (3+5*4 inputs to AND gates)+1 OR gate+6 inputs to the OR gate=36.

		\bar{x}_1				Row pattern	x_1				Row pattern
		\bar{x}_3	\bar{x}_2	x_3	x_2	\bar{x}_3	\bar{x}_3	\bar{x}_2	x_3	x_2	\bar{x}_3
\bar{x}_4	\bar{x}_5	d	0	0	0	0	0	d	0	0	0
	x_5	1	0	0	1	$\bar{g} = \bar{x}_3$	0	0	0	1	$g_2 = x_2\bar{x}_3$
x_4		0	1	d	0	$g = x_3$	1	0	1	0	$g_3 = \bar{x}_2 \oplus x_3$
	\bar{x}_5	1	0	0	1	$\bar{g} = \bar{x}_3$	1	0	0	d	$g = \bar{x}_3$
Col pattern		$h = x_4 \oplus x_5$	$h_2 = x_4x_5$	0	h		$h_3 = x_4$	0	$h_2 = x_2x_4$	h	

Table 1: K-map for Problem 4.

		\bar{x}_1				x_1			
		\bar{x}_3	\bar{x}_2	x_3	x_2	\bar{x}_3	\bar{x}_2	x_3	x_2
\bar{x}_4	\bar{x}_5	d	0	0	0	0	d	0	0
	x_5	1	0	0	1	0	0	0	1
x_4		0	1	d	0	1	0	1	0
	\bar{x}_5	1	0	0	1	1	0	0	d

Table 2: K-map for Problem 4.