

Logic minimization: Minimum-cost circuits

Vikas Dhiman for ECE275

September 16, 2022


1 A few more Boolean problems

Example 1. *Simplify the following Boolean expression:*

$$f = x_1\bar{x}_3\bar{x}_4 + x_2\bar{x}_3\bar{x}_4 + x_1\bar{x}_2\bar{x}_3$$

Example 2. *Using algebraic manipulation to prove that:*

$$x + yz = (x + y)(y + z)$$

 

Example 3. *Design a three-way light control*


2 Logic minimization

A general optimization criteria for multi-level logic are to Minimize some combination of:

1. Area occupied by the logic gates and interconnect;
2. the Critical Path Delay of the longest path through the logic;
3. the Degree of Testability of the circuit, measured in terms of the percentage of faults covered by a specified set of test vectors, for an appropriate fault model (Eg., single stuck faults, multiple stuck faults, etc.);
4. Power consumed by the logic gates.

In this course, we will start with two-level multi-input circuits and a criteria based on the number of gates/transistors/diodes.

3 Programmable Logic Arrays

 

4 Two-level circuits

The cost that we are going to consider in this class depend upon:

1. Number of gates.
2. Number of input to the gates.

More gates need more transistors, more area on the chip. More-inputs the gate need more transistors within each gate. Number of gate inputs can be considered secondary criterion to the number of gates.

Example 4. Find the cost of the following Boolean expression $X = \overline{A}\overline{B}C + ABC\overline{C} + AB\overline{C}$.