

Electrical noise could cause a problem

$$\begin{aligned} NM_H &= V_{OH} - V_{IH} \\ NM_L &= V_{IL} - V_{OL} \end{aligned} \quad \begin{array}{l} \text{NOISE} \\ \text{MARGIN} \end{array}$$

These parameters describe how much noise can be tolerated before causing trouble.

Example: Low-voltage CMOS logic family


Parameters:

$$\begin{aligned} V_{DD} &= 3.3 \text{ V} \\ V_{IL} &= 0.9 \text{ V} \\ V_{IH} &= 1.8 \text{ V} \\ V_{OL} &= 0.36 \text{ V} \\ V_{OH} &= 2.7 \text{ V} \end{aligned}$$

Find noise margin:


$$\begin{aligned} NM_L &= V_{IL} - V_{OL} \\ &= 0.9 - 0.36 = 0.54 \text{ V} \end{aligned}$$
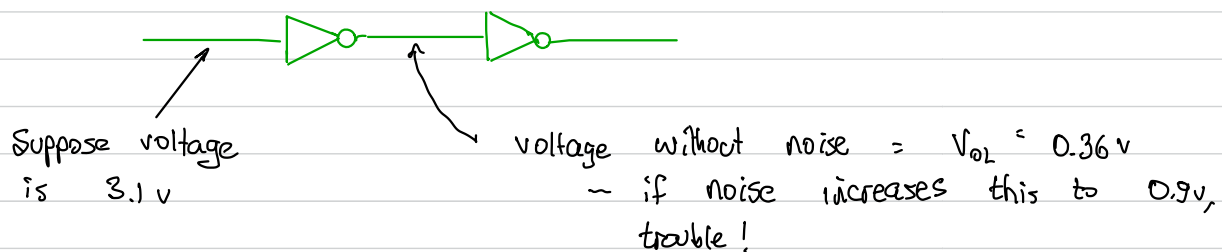
$$\begin{aligned} NM_H &= V_{OH} - V_{IH} \\ &= 2.7 - 1.8 = 0.9 \text{ V} \end{aligned}$$



Combinational Circuit Design (Chapter 2)


Composition of a simple logic circuit

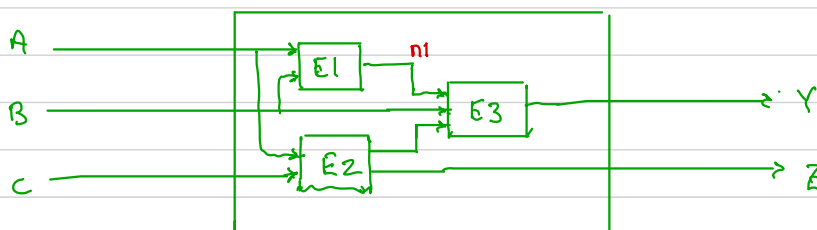

The circuit is generally described in terms of elements and nodes

- E_1, E_2, E_3 are elements (which can themselves be a logic circuit)
- a node is connection between elements (i.e., a wire!)
- Node types
 - input nodes A, B, C ; output nodes (Y, Z) .
 - internal nodes, like n_1 .

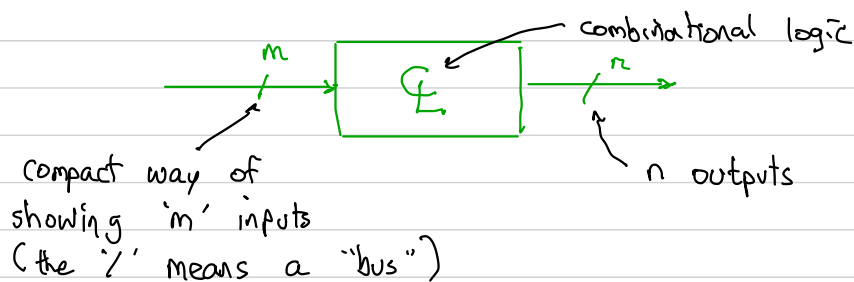The generic symbol for a combination circuit




Definition of a combinational circuit.

- all of E_1, E_2 , etc., must be combinations!
- Nodes are all either inputs or outputs; if an output, it connects to the output of just one other circuit element.



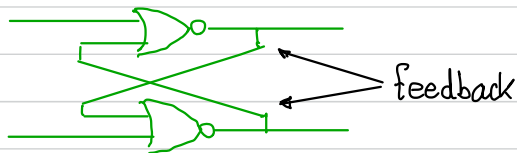- No cyclic path (i.e., no feedback path)



Boolean algebra

Boolean equations operate on binary variables, so are ideal for describing digital logic circuits.

Terminology

There is much in common with conventional algebra, but with some important new terms:

- complement
- literal
- minterm
- maxterm ... and more

A literal

- is defined as a single Boolean variable or its complement

E.g., A, \bar{A}, B, \bar{B} (each are one literal)

$A + \bar{B}C \rightarrow$ is an expression containing 3 literals

$A + \bar{B}C\bar{A} \rightarrow$ has 4 literals ('A' used twice)

True form of a literal: A (not complemented)

Complementary form: \bar{A}

Product term

- can be a single literal
- or the ANDing of 2 or more literals

E.g.,

- A
- $AB\bar{C}\bar{D}$
- $AB\bar{C} + \bar{D}$ (not a product term overall, but ORing of two product terms)

- also called an implicant.

A minterm

A product term that contains all system variables in either true or complementary form.

2-variable system

minterms: $\left. \begin{array}{l} \bar{A}\bar{B} \\ \bar{A}B \\ A\bar{B} \\ AB \end{array} \right\} \begin{array}{l} \text{all 4} \\ \text{combinations} \end{array}$

3-variable system

minterms: $\left. \begin{array}{ll} \bar{A}\bar{B}\bar{C} & A\bar{B}\bar{C} \\ \bar{A}\bar{B}C & A\bar{B}C \\ \bar{A}B\bar{C} & AB\bar{C} \\ \bar{A}BC & ABC \end{array} \right\} \begin{array}{l} \text{all 8} \\ \text{combinations} \end{array}$