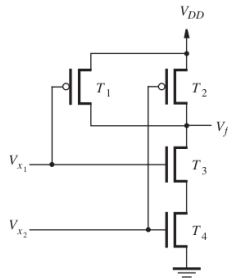


# CMOS circuit review

Vikas Dhiman for ECE275

October 24, 2022


## 1 CMOS gate review



(a) Circuit


$x_1$	$x_2$	$T_1$	$T_2$	$T_3$	$T_4$	$f$
0	0	on	on	off	off	1
0	1	on	off	off	on	1
1	0	off	on	on	off	1
1	1	off	off	on	on	0

(b) Truth table and transistor states

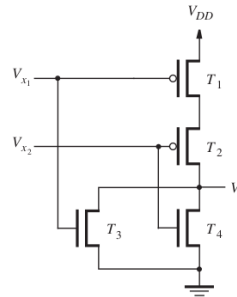

$x_1$	$x_2$	$T_1$	$T_2$	$T_3$	$T_4$	$f$
0	0	on	on	off	off	1
0	1	on	off	off	on	0
1	0	off	on	on	off	0
1	1	off	off	on	on	0

CMOS NOR gate

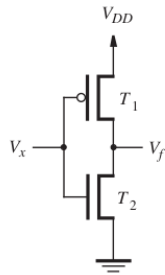


(a) Circuit

$x$	$T_1$	$T_2$	$f$
0	on	off	1
1	off	on	0

(b) Truth table and transistor states

CMOS NOT gate

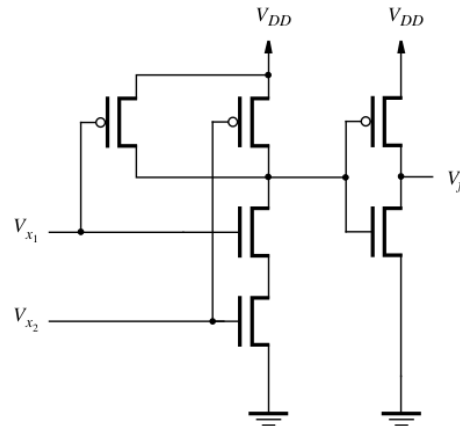

CMOS AND gate

**Example 1** Derive the CMOS complex gate that implements  $f = \overline{x_1 x_2 + x_3 x_4 + x_5}$ .

**Problem 1** Derive the CMOS complex gate that implements  $f = \bar{x}_1 \bar{x}_2 x_3 + \bar{x}_1 x_2 \bar{x}_3 + x_1 \bar{x}_2 \bar{x}_3 + x_1 x_2 x_3$ .