

# Analog details behind the digital abstraction

Vikas Dhiman for ECE275


October 17, 2022

Some of the material is out of the textbook. Additional resources include Appendix B of Brown and Vranesic book, “Fundamentals of digital logic.”

## 1 Objectives

1. Describe how tri-state and open-collector outputs are different from totem-pole outputs
2. Compute noise margin of one device driving the same time
3. Understand timing diagrams, gate delays and critical path
4. Design Hazard-free two level circuits

## 2 Logic levels and Noise Margins

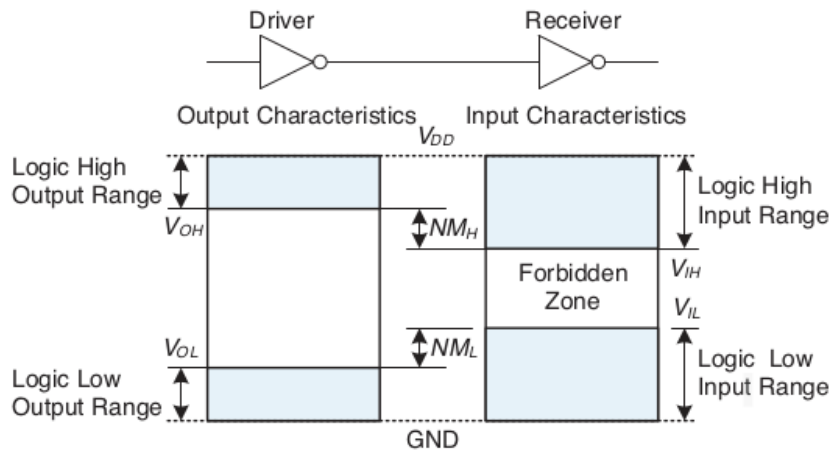

**Definition 1** (Supply Voltage ( $V_{DD}/V_{CC}/V_{SS}$ )).


**Definition 2** (Ground Voltage ( $V_{GND}$ )).

**Definition 3** (Input high ( $V_{IH}$ ) and Input Low ( $V_{IL}$ ) of a gate).

**Definition 4** (Output high ( $V_{OH}$ ) and Output low ( $V_{OL}$ ) of gate).

**Definition 5** (Positive logic and Negative logic).

**Definition 6** (Noise margins ( $NM_L$  and  $NM_H$ ) of a channel).

 

**Example 1.**

If  $V_{DD} = 5V$ ,  $V_{IL} = 1.35V$ ,  $V_{IH} = 3.15V$ ,  $V_{OL} = 0.33V$  and  $V_{OH} = 3.84V$  for both the “inverters”, then what are the low and high noise margins? Can the circuit tolerate 1V of noise at the channel?


### 3 Semiconductors and Doping

Not in syllabus but good to know

Elements recognized as metalloids V • T • E



	13	14	15	16	17
2	B Boron	C Carbon	N Nitrogen	O Oxygen	F Fluorine
3	Al Aluminium	Si Silicon	P Phosphorus	S Sulfur	Cl Chlorine
4	Ga Gallium	Ge Germanium	As Arsenic	Se Selenium	Br Bromine
5	In Indium	Sn Tin	Sb Antimony	Te Tellurium	I Iodine
6	Tl Thallium	Pb Lead	Bi Bismuth	Po Polonium	At Astatine

 Commonly recognized (86–99%): B, Si, Ge, As, Sb, Te  
 Irregularly recognized (40–49%): Po, At  
 Less commonly recognized (24%): Se  
 Rarely recognized (8–10%): C, Al  
 (All other elements cited in less than 6% of sources)  
 Arbitrary metal-nonmetal dividing line: between Be and B, Al and Si, Ge and As, Sb and Te, Po and At




## 4 MOSFET: Metal Oxide Field Effect Transistors


Not in syllabus but good to know

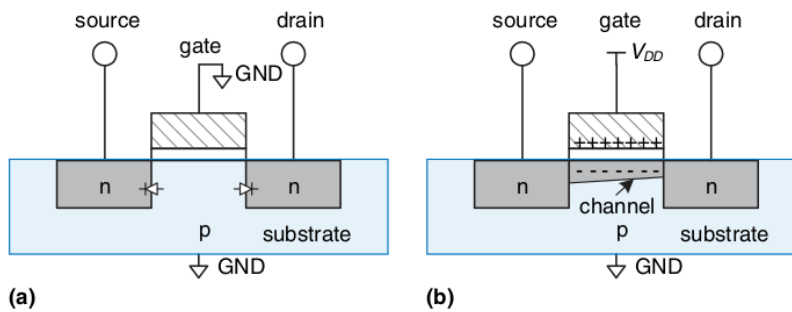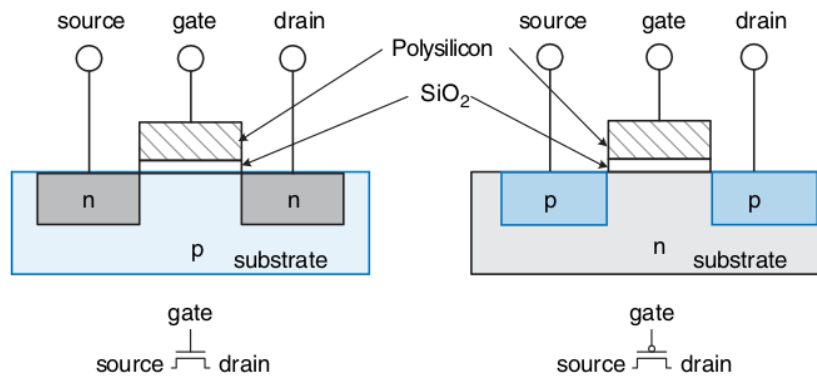


## 5 DC Transfer characteristic

 


(a) NMOS NOT gate

 


(b)  $V_x = 5\text{ V}$

 


(a)

 

(b)

 

(a) NMOS transistor

 

(b) PMOS transistor

**Example 2.** Draw a *NOT* gate using *nMOS* transistors.

**Example 3.** Draw a *NOT* gate using *pMOS* transistors.

**Remark 1.** *nMOS* transistors pass 0's well (output between 0 and  $V_{DD} - V_t$ ). *pMOS* transistors pass 1's well (output between  $V_t$  and  $V_{DD}$ ).

**Example 4.** *Draw CMOS NOT Gate.*

**Example 5.** *Draw a two input CMOS NAND Gate*


**Definition 7** (Negative logic).

**Example 6.** *Analyze the above circuit under negative logic.*


**Example 7.** *Draw a three input NAND using CMOS.*

**Example 8.** *Draw a three input NOR using CMOS.*

 **Example 9.** Draw a two input AND gate using CMOS.



## 5.1 Gates with floating output

 

**Definition 8** (Transmission gate). Draw a schematic of transmission gate and truth table for transmission gate. What is its commonly used symbol?

**Definition 9** (Tristate buffer). *What is tristate buffer? Draw it's symbol and truth table? Where is it used?*

**Example 10.** *Draw a Multiplexer using transmission gates.*

**Example 11.** *Draw a Multiplexer using tristate buffers.*

**Definition 10** (Totem-pole). *Draw a Push-pull (or Totem-pole) output NAND gate using CMOS. Can you connect this gate to a shared bus?*

**Definition 11** (Tristate). *Draw a Tristate output NAND gate using CMOS with an output enable (OE) input. Can you connect this gate to a shared bus?*



**Definition 12** (Open-collector). *Draw a open-collector output NAND gate. Can you connect this gate to a shared bus?*

## 6 Verilog truth tables

Table 11-11—Bitwise binary AND operator

&	0	1	x	z
0	0	0	0	0
1	0	1	x	x
x	0	x	x	x
z	0	x	x	x


Table 11-12—Bitwise binary OR operator

	0	1	x	z
0	0	1	x	x
1	1	1	1	1
x	x	1	x	x
z	x	1	x	x

## 7 Timing diagrams and propagation delays

**Example 12** (Timing diagram). *Draw a timing diagram for an ideal NAND gate.*


## 7.1 Delays

 

**Definition 13** (Propagation delay ( $t_{pd}$ )).


**Definition 14** (Contamination delay ( $t_{cd}$ )).

## 7.2 Paths

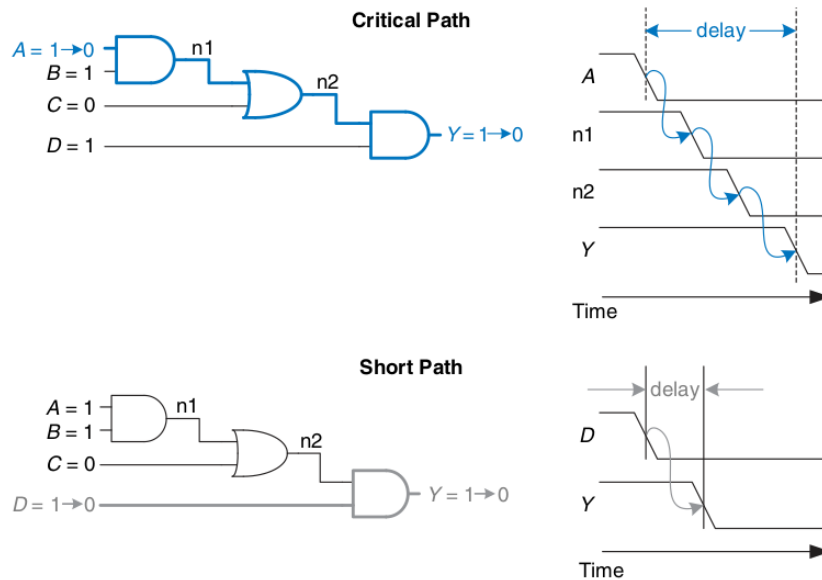

**Example 13.** Find the propagation delay of the circuit above given that propagation delay of each gate is 100ps add contamination delay of 60ps.

## 8 Glitches or Hazards

 

**Definition 15** (Glitch or Hazard).

**Example 14.** Design a circuit that fixes the glitch in the above circuit (also known as *glitch-free* or *hazard-free* circuit).