

# ECE275 Midterm 1 Fall 2022

Instructor: Vikas Dhiman ([vikas.dhiman@maine.edu](mailto:vikas.dhiman@maine.edu))

September 29, 2022

Student Name:

Student Email:


## 1 Instructions

- Time allowed is 50 minutes. (This sample exam might be lengthier than the actual exam. )
- In order to minimize distraction to your fellow students, you may not leave during the last 10 minutes of the examination.
- The examination is closed-book. One 8x11in cheatsheet is allowed.
- Non-programmable calculators are permitted.
- The maximum number of marks is 100, as indicated; the midterm examination amounts 10% toward the final grade.
- Please use a pen or heavy pencil to ensure legibility.
- Please show your work; where appropriate, marks will be awarded for proper and well-reasoned explanations.

**Problem 1.** *Number conversions:*

1. Use repeated division to convert  $230_{10}$  to octal representation (5 marks).
2. What is the value of  $19D_{16}$  in base 10 (5 marks).
3. A 6-bit two's complement number is  $100011_2$ . Convert it to (signed) decimal (5 marks).
4. Represent  $-23_{10}$  in two's complement binary notation (5 marks).

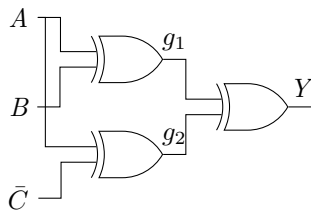**Problem 2.** *Consider the circuit below*



*By algebraic manipulation, prove or disprove that  $Y = \bar{B}\bar{C} + BC$  (10 marks).*

**Problem 3.** Use the following 5-variable K-map for  $F(A, B, C, D, E)$ , and find a minimal SOP expression for  $F$  (15 marks)


DE \ BC	BC			
	00	01	11	10
00	1			1
01	1	1		1
11		1		
10		1	1	

$A=0$

DE \ BC	BC			
	00	01	11	10
00		1	1	
01	1	1		1
11		1		
10		1	1	

$A=1$

**Problem 4.** Use bubble-pushing and/or algebra to find an SOP expression for  $Y$  in the circuit below. If you use bubble-pushing, draw an equivalent circuit beside the given circuit (5 marks).

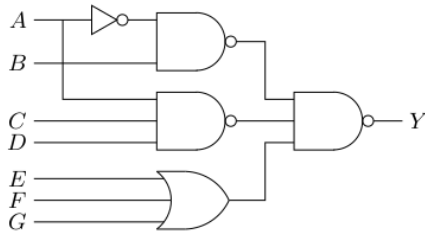

**Problem 5.** Consider the function  $Y$  given below.

$$Y(A, B, C, D) = \sum m(0, 3, 5, 7, 8, 14) + d(2, 12, 15)$$

1. Draw a K-maps to derive a minimum SOP and POS expressions for  $Y$ . Indicate all essential prime implicants for  $Y$  or  $\bar{Y}$  in your K-maps (20 marks).
2. Sketch a two-level NOR-NOR circuit for  $Y$ . Assume that  $A$ ,  $B$ ,  $C$ , and  $D$  are available in true and complementary forms (5 marks).
3. Write  $Y$  in Product of sums (POS) canonical form (5 marks).

**Problem 6.** Design a minimal SOP circuit to add two two-bit unsigned numbers. Denote the two bits of first number as  $A_1A_0$  and the two bits of second number as  $B_1B_0$ . The result will be a 2-bit sum  $S_1S_0$  and a carry  $C$ . Start with filling out the following truth table (3 example rows are provided) and then use K-maps to find minimal SOP for  $S_1$ ,  $S_0$  and a single carry bit  $C_1$  (20

	$A_1$	$A_0$	$B_1$	$B_0$	$C_1$	$S_1$	$S_0$
	0	0	0	0			
	0	0	0	1			
	0	0	1	0			
	0	0	1	1			
	0	1	0	0			
	0	1	0	1	0	1	0
	0	1	1	0			
marks).	0	1	1	1			
	1	0	0	0			
	1	0	0	1			
	1	0	1	0			
	1	0	1	1			
	1	1	0	0			
	1	1	0	1	1	0	0
	1	1	1	0			
	1	1	1	1	1	1	0